

# Electrical Engineering

Electronics and Communication Engineering

## NETWORK THEORY



Lecture No. 01

BASICS OF

NETWORK THEORY




By- Pankaj Shukla sir



1. Basics
2.  $q(t)$ ,  $i(t)$ ,  $v(t)$
3.  $P(t)$ ,  $w(t)$
4. Power absorbing
5. Power delivers
- 6.



### Basics of Network theory

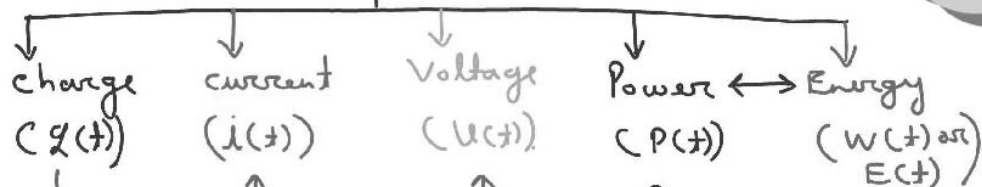


[Basic Building block of N/w theory]



Charge ( $q(t)$ )  $\rightarrow$  It is a bipolar.  $\begin{bmatrix} \oplus \\ \ominus \end{bmatrix}$

- It is the most fundamental quantity.
- Charge exposure can be felt.

charge has two electrical effects.

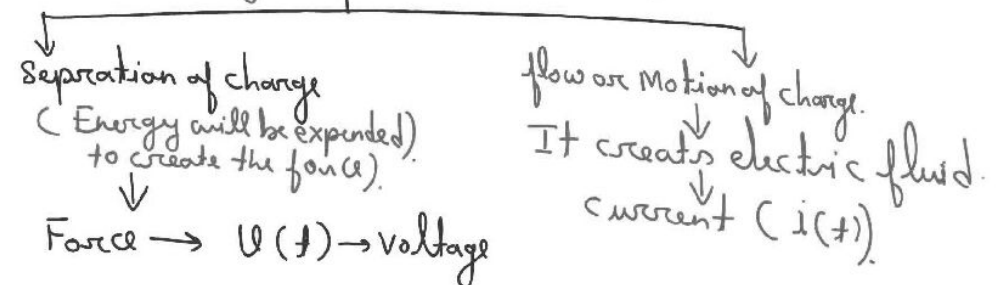



$P(t) = \frac{dW(t)}{dt} \rightarrow$  Rate of change of energy wrt time  
 $\rightarrow$  Slope of  $W(t)$  Vs 't' graph.  
 $W(t) = \int P(t) \cdot dt \rightarrow$  Area under the curve  
 $[P(t) \text{ Vs 't'}]$

Topic-02: Concept of Absorbing & Delivering Power.  

**Network.**

↓

- It is a just connection of electrical elements.
- Minimum requirement of element to form a N/w is 2.

**Circuit.**

↓

- It is also the connection of electrical elements but with certain fixed requirements.
- ① It must have atleast one Independent Source
- ② It must have atleast one closed path.

Note: "All circuits are always Network but all networks are not necessarily to be a circuit"

Condition for the flow of current:  
 There are three-must condition:  
 Condition 01: There must be atleast one Independent Source in the N/w or circuit.  
 Condition 02: There must be atleast one closed Path.  
 Condition 03: There must be a return path also.

$X \& Y \rightarrow$  can be any element.

$P_X \rightarrow$  Absorbing Power  
 $P_X = (V \cdot I) \rightarrow \oplus \text{ or } \ominus$

It is Independent of the Sign of  $V \& I$ .

$P_Y \rightarrow$  Delivering Power  
 $P_Y = V \cdot I \rightarrow \oplus \text{ or } \ominus$

It is independent of Sign of  $V \& I$ .

[ • In a whole electrical circuit: ]



(1)  $\left[ \sum P_T \text{ or } \sum W_T = 0 \right]$   
---→ Energy or Power conservation principle.  
or  
→ Energy can not be created or can not be destroyed.

(2) In a whole circuit,  
 $\left[ \sum P_{T(\text{Actual Deliver})} = \sum P_{T(\text{Actual absorb})} \right]$

[



@ pankajshukla sir pw

(telegram)

Thank you

**GW**  
*Soldiers!*

