

# Electrical Engineering

Electronics and Communication Engineering

## NETWORK THEORY



Lecture No. 01

BASICS OF

NETWORK THEORY


By - Pankaj Shukla sir

### Topics to be Covered

1. Basics
2.  $q(t)$ ,  $i(t)$ ,  $v(t)$
3.  $P(t)$ ,  $w(t)$
4. Power absorbing
5. Power delivering
- 6.



### Basis of Network theory

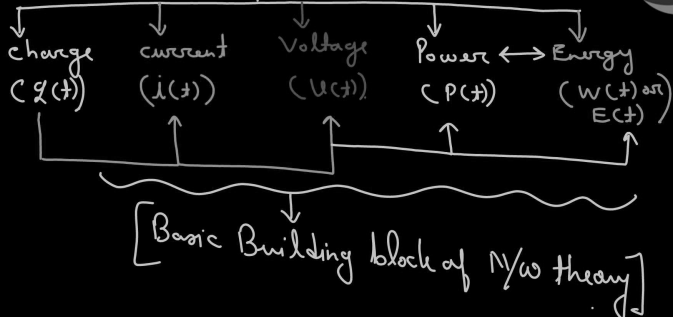

charge ( $q(t)$ )  $\rightarrow$  It is a bipolar.  $\begin{matrix} \oplus \\ \ominus \end{matrix}$

- It is the most fundamental quantity.
- Charge exposure can be felt.

charge has two electrical effects.

Separation of charge  
(Energy will be expended to create the force).  
 $\downarrow$   
Force  $\rightarrow v(t) \rightarrow$  Voltage

flow or Motion of charge.  
It creates electric field.  
 $\downarrow$   
current ( $i(t)$ )





[  $p(t) = \frac{dw(t)}{dt} \rightarrow$  Rate of change of energy wrt time  $\left( \frac{P}{W} \right)$   
 $\rightarrow$  Slope of  $w(t)$  Vs 't' graph.  
 $w(t) = \int p(t) \cdot dt \rightarrow$  Area under the curve  
 $[P(t) \text{ Vs } t]$  ]

[ Topic-02: Concept of Absorbing & Delivering Power. ]  $\left( \frac{P}{W} \right)$

**Network.**

↓

- It is a just connection of electrical elements.
- Minimum requirement of element to form a N/w is 2.

**Circuit.**

↓

- It is also the connection of electrical elements but with certain fixed requirements.
- ① It must have atleast one Independent Source
- ② It must have atleast one closed path.

Note: "All circuits are always Network but all networks are not necessarily to be a circuit"

[ Condition for the flow of current. ]  $\left( \frac{P}{W} \right)$

There are three-must condition:

Condition 01: There must be atleast one Independent Source in the N/w or circuit.

Condition 02: There must be atleast one closed path.

Condition 03: There must be a return path also.

[ • ]  $\left( \frac{P}{W} \right)$

a  $\uparrow$  I  $\rightarrow \oplus$  or  $\ominus$

$\downarrow$  I  $\leftarrow \oplus$  or  $\ominus$

b

$P_x \rightarrow$  Absorbing Power

$P_x = (V \cdot I) \rightarrow \oplus$  or  $\ominus$

It is Independent of the sign of  $V$  &  $I$ .

a  $\uparrow$  I  $\rightarrow \oplus$  or  $\ominus$

$\downarrow$  I  $\leftarrow \oplus$  or  $\ominus$

b

$P_y \rightarrow$  Delivering Power

$P_y = V \cdot I \rightarrow \oplus$  or  $\ominus$

It is independent of sign of  $V$  &  $I$ .

$X \& Y \rightarrow$  can be the element.

